
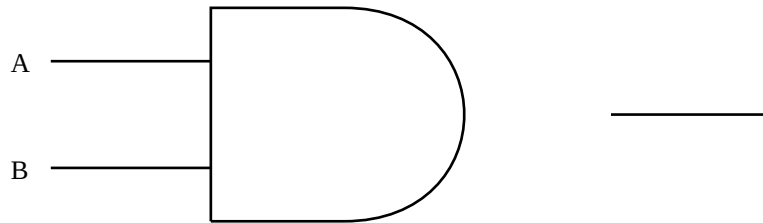


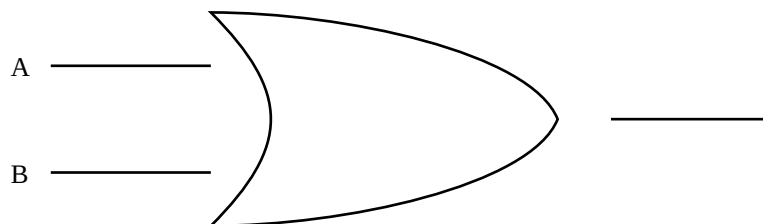Basic Logic Gates - Proper Diagrams and Truth Tables




AND Gate

A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1



OR Gate


A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

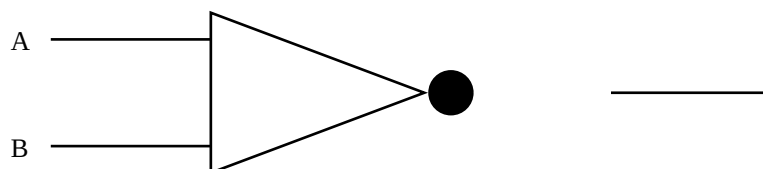

NOT Gate


A	$Y=A'$
---	--------

0	1
1	0

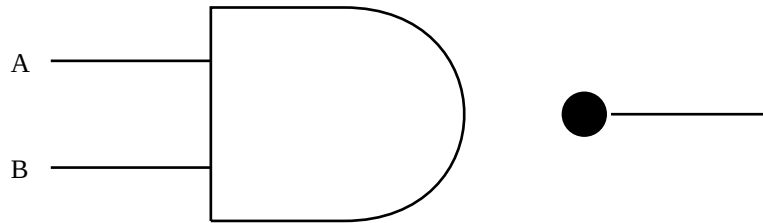


NAND Gate

A	B	$Y=(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

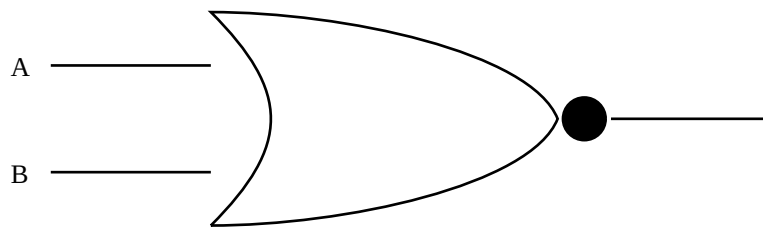

NOR Gate

A	B	$Y=(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

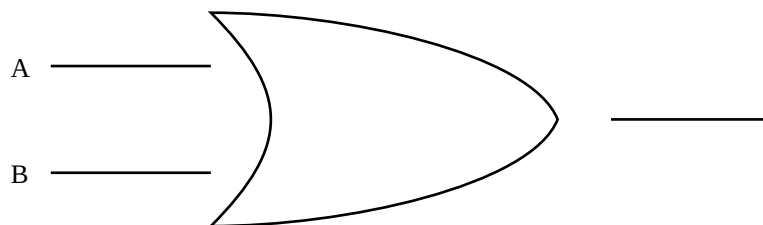

XOR Gate

A	B	$Y=A\oplus B$
0	0	0

0	1	1
1	0	1
1	1	0